Week 1 Notes

Transient

-
-

Simple RC transient Notes

- THERE IS NO CURRENT FLOWING THROUGH THE CAPACITOR